

Github url:

<https://github.com/Almo-o/Computer-Organization-and-Assembly/tree/main/Assignment-2>

Brief Description:

The register file is designed with two read ports and one write port to enable simultaneous data access. Two independent read address decoders fetch data from two registers via multiplexers, while a write decoder selects the target register for writing when the write-enable signal is active.

ALU: Components- a 4-bit adder, a multiplexer, and control signals (S1,S0,Cin). The MUX selects between inputs like B, -B (complement of B), 0000, or 1111, which are fed into the adder along with `A` and `Cin`. Operations such as addition, subtraction (via 2's complement), increment, decrement, and transfer are achieved by configuring the control signals to manipulate the adder's inputs dynamically. This design efficiently reuses hardware components for multiple functions.

Screenshots:





