

Github url: <https://github.com/Almo-o/Computer-Organization-and-Assembly/tree/main>

1. $Q = 0, Q' = 1$

2. Characteristics of each flip flop

SR flip flop:

Inputs: S (set) and R (reset)

Outputs: Q (current state) and Q' (complement Q)

Characteristic Table:

Q _n	S	R	Q _{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	x
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	x

D flip flop:

Single input D

Outputs: Q (current state) and Q' (complement Q)

Characteristic Table:

Q _n	D	Q _{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

JK flip flop:

Inputs: J and K

Outputs: Q (current state) and Q' (complement Q)

Characteristic Table:

Q _n	J	K	Q _{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

T flip flop:

Single input T:

Outputs: Q (current state) and Q' (complement Q)

Characteristic Table:

Q _n	T	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

3. Excitation tables

Sr flip flop

Q(t)	Q(t+1)	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

D flip flop

Q(t)	Q(t+10)	D
0	0	0
0	1	1
1	0	0
1	1	1

JK flip flop

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

T flip flop

Q(t)	Q(t+10)	T
0	0	0
0	1	1
1	0	1
1	1	0

4. 5 latches

5. 32 states

6. design a two-bit up/down counter using the input direction such that when direction = 0, the system decrements (00 -> 11 -> 10 -> 01 -> 00) and when direction = 1, the system increments (00 -> 01 -> 10 -> 11 -> 00)

State table

Current state (Q1,Q0)	Input (direction)	Next State
00	0	11
00	1	01
01	0	00
01	1	10
10	0	01
10	1	11
11	0	10
11	1	00

K-map

Q1'

	00	01	11	10
0	1	0	1	0
1	0	1	0	1

Boolean expression:

$$= (Q1 \text{ XNOR } Q0) \text{ XOR Direction}$$

K-map


Q0'

	00	01	11	10
0	1	0	0	1
1	1	0	0	1


Boolean expression : relies only on Q0 being 0

$$= \neg Q0$$

Circuit for Two-bit-up/down-counter

 

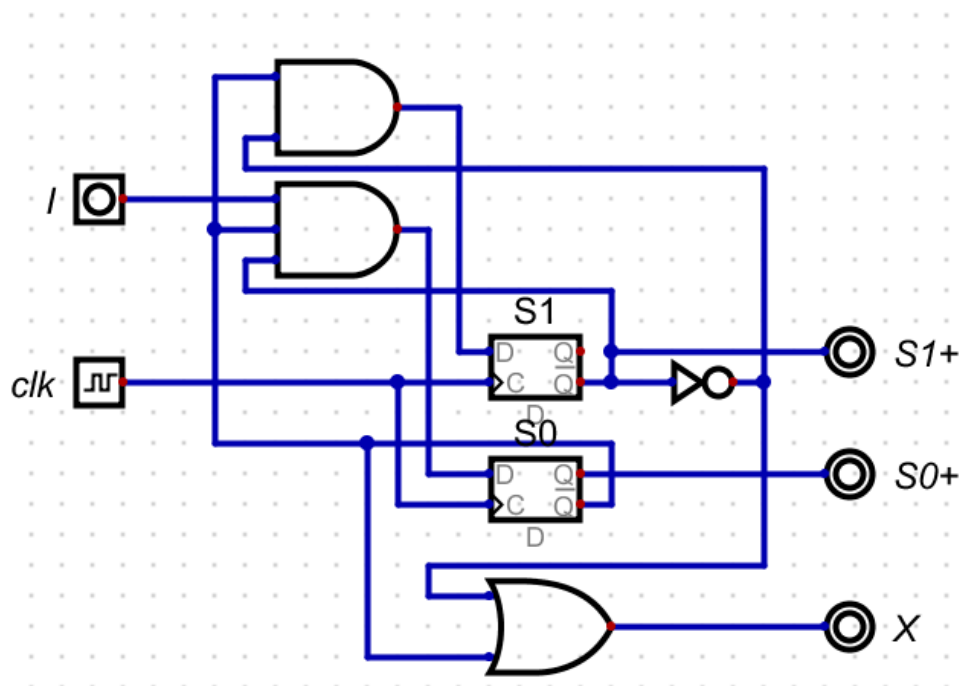7. The three Boolean expressions below represent the next state bits, $S1'$ and $S0'$, and the output bit, X , based on the current state, $S1$ and $S0$, and the input I . Draw the logic circuit for the state machine including the latches and output circuitry. Label all signals.



8.

State Truth Table

Current state (S1,S0)	Input (direction)	Next State
00	0	01
00	1	10
01	0	11
01	1	10
10	0	11
10	1	00
11	0	10
11	1	01

Output table

Current State	Output
00	1
01	1
10	0
11	1

8.b)

Current state (S1,S0)	Input (direction)	Next State
00	0	01
00	1	00
01	0	01
01	1	10
10	0	00
10	1	01

Output table

Current State	Output
00	0
01	1
10	1

9. Design a state machine to detect the bit pattern "110" in a stream of bits

